

EE227 Digital Logic Design

Monday, July 20, 2020

Course Instructor

Engr. Amir Zahoor

Engr. Muhammad Abdullah

Mr. Waheed Ahmad

Serial No:

Final Term Exam

Spring Semester 2020

Max Time:

3 Hours

Max Marks: 85

Exam Weight (Out of 100). 50

Roll No

Section

Guidelines for Submission:

1. You should submit only one PDF document and **all text should be handwritten**. Equations, figures should be hand draw.
2. You must submit your solution before due time via **Google Classroom/Slate**. Submissions submitted after the due time shall not be considered.
3. If you don't finish every part of a question, don't worry! You can still submit what you've done to get marks based on your efforts.
4. In case of copied or plagiarized solutions in exam Or If a student provided help to another student during exam both will be awarded "F" grade and it will affect the student CGPA.
5. Viva of any student can be conducted by the instructor after conducting an online exam in case of any doubt.
6. This document should be submitted through LMS (**Google Classroom**). But in worst case, you can email it within the deadline.

Question	1	2	3	4	5	6	Total
Points	10	15	15	15	15	15	85
Score							

Question No. 1 (10)

Convert each of the following expressions into sum of products and product of sums:

a) $(u + xw)(x + u'v)$

b) $x' + x(x + y')(y + z')$


Question No. 2 (15)

Using Truth table and Karnaugh Maps, design a 7-segment Display combinational circuit. The circuit receives a BCD number input ABCD and displays decimal number 0 to 9 on a single digit 7-segment display. The six invalid combinations in BCD should be treated as don't care conditions.

 Question No. 3 (15)

Analyze the given sequential circuit and answers following;

- Write down the state equations?
- Write down the first form of state table?
- Write second form of State Table?
- Draw the state diagram?



Question No. 4

(15)

Design a counter with T flip-flops that goes through the following binary repeated sequence: 0, 1, 3, 7, 6, 4. (You can consider 010 and 101 as don't care conditions)
Draw the logic diagram.

Question No. 5

(15)

Consider the following state table obtained from state transition diagram of a circuit with 2 inputs (x and y) and 1 output (F).

State	Next State				Output (F)			
	$xy = 00$	$xy = 01$	$xy = 10$	$xy = 11$	$xy = 00$	$xy = 01$	$xy = 10$	$xy = 11$
<i>a</i>	<i>b</i>	<i>d</i>	<i>c</i>	<i>b</i>	0	1	1	0
<i>b</i>	<i>a</i>	<i>c</i>	<i>f</i>	<i>d</i>	1	0	1	1
<i>c</i>	<i>b</i>	<i>d</i>	<i>c</i>	<i>b</i>	0	1	1	0
<i>d</i>	<i>b</i>	<i>d</i>	<i>a</i>	<i>b</i>	0	1	1	0
<i>e</i>	<i>b</i>	<i>c</i>	<i>a</i>	<i>b</i>	0	1	1	0
<i>f</i>	<i>c</i>	<i>d</i>	<i>g</i>	<i>f</i>	0	1	1	0
<i>g</i>	<i>a</i>	<i>b</i>	<i>d</i>	<i>g</i>	1	1	0	1

- (a) Reduce the number of states in the state transition diagram
(b) Draw the reduced state transition diagram

Marks: 10

Marks: 5

(15)

For your convenience, the block diagram of FSM and sample input ‘X’ and sample output ‘Y’ is shown below;

