

EE227 – Digital Logic Design

Assignment 8

Spring 2020

Instructor Name: Engr. Amir Zahoor


Instructions for Submission:

- .
- Partially or fully **copied assignments** will be marked as **zero**.
- You should submit only one PDF document and all text should be hand written. Equations, figures can only be hand written (all figures/equations can be pasted as images inside that document).
- Only **handwritten** solution.
- Late submissions are not allowed.
- Viva of any student can be conducted by the instructor after conducting an online exam in case of any doubt.
- You can submit your assignment **during Google Classroom only**.

Question Number 1

Design the sequential circuit for the following state diagram with the help of;

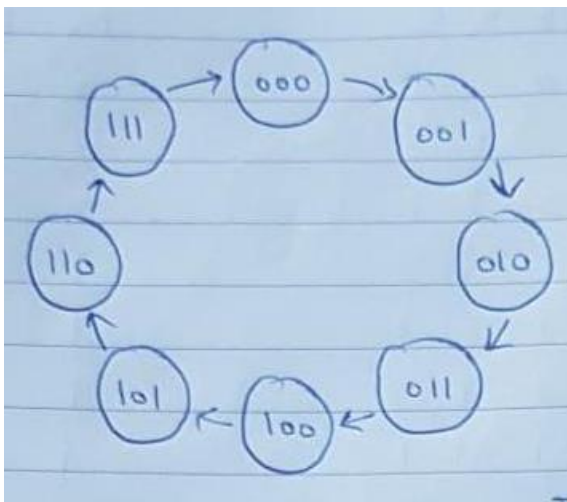- a) D- Flip Flop
- b) JK- Flip Flop
- c) T- Flip Flop



Question Number 2

Draw the Universal Shift Register for 4-bits.

Good Luck