



EE227 – Digital Logic Design

Quiz No. 3

Name: _____

Roll No.: _____

Section: **BSCS17-E**

Marks: 10

Submission Guidelines:

1. You should submit only one PDF document and all text should be handwritten. Equations, figures should be hand draw.
2. You must submit your solution before due time via [Google Classroom](#). Submission submitted after the due time shall not be considered.
3. If you don't finish every part of a question, don't worry! You can still submit what you've done to get marks based on your efforts.
4. In case of copied or plagiarized solutions in exam Or If a student provided help to another student during Quiz both will be awarded "0" Marks.
5. Viva of any student can be conducted by the instructor in case of any doubt.

Question#02 (10 Marks)

Consider the function F with 3 inputs:

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Draw a circuit for F using 2-to-1 multiplexer and few additional gates as possible.